

SOLUTIONS

1. (a) Given $I_a=1/\underline{60^\circ}$, $I_b=1/\underline{-60^\circ}$, $I_c=0$, find the sequence components (the 012 components corresponding to the a-phase currents).
(a) Find the 012 components corresponding to the c-phase.
(b) Sum the 012 components corresponding to the c-phase to see if they sum to 0.

Part a)

$$\begin{aligned} I_1 &= \frac{1}{3}(I_a + aI_b + a^2I_c) \\ &= \frac{1}{3}(1\angle 60^\circ + 1\angle 60^\circ + 0) \\ &= 0.667\angle 60^\circ \\ I_2 &= \frac{1}{3}(I_a + a^2I_b + aI_c) \\ &= \frac{1}{3}(1\angle 60^\circ + 1\angle 180^\circ + 0) \\ &= 0.333\angle 120^\circ \\ I_0 &= \frac{1}{3}(I_a + I_b + I_c) \\ &= \frac{1}{3}(1\angle 60^\circ + 1\angle -60^\circ + 0) \\ &= 0.333\angle 0^\circ \end{aligned}$$

Part b)

$$\begin{aligned} I_{c1} &= aI_1 = 0.667\angle 180^\circ \\ I_{c2} &= a^2I_2 = 0.333\angle 360^\circ \\ I_{c0} &= I_0 = 0.333\angle 0^\circ \end{aligned}$$

Part c)

$$\begin{aligned} I_c &= I_{c1} + I_{c2} + I_{c0} \\ &= -0.667 + 0.333 + 0.333 \cong 0 \end{aligned}$$

2. A Y-connected solidly grounded voltage source with unbalanced voltage is applied to a balanced line and load. Assume that there is no mutual coupling between phases. The load is connected delta.

Data for the problem is as follows:

Voltage source: $V_{ag}=277/_0^\circ$, $V_{bg}=260/_-120^\circ$, $V_{cg}=295/_115^\circ$

Load impedance : $30/_40^\circ$.

Line impedance: $1/_85^\circ$.

- (a) Compute sequence source voltages.
- (b) Compute the 012 currents in the line.
- (c) Compute the abc currents in the line.

Note, when converting the delta load to wye, it must remain **ungrounded**.

Part a)

$$\begin{aligned}V_1 &= \frac{1}{3}(V_{ag} + aV_{bg} + a^2V_{cg}) \\&= \frac{1}{3}(277\angle 0^\circ + 260\angle 0^\circ + 295\angle -5^\circ) \\&= 277.1\angle -1.772^\circ \text{ volts} \\V_2 &= \frac{1}{3}(V_{ag} + a^2V_{bg} + aV_{cg}) \\&= \frac{1}{3}(277\angle 0^\circ + 260\angle 120^\circ + 295\angle 235^\circ) \\&= 9.218\angle 216.59^\circ \text{ volts} \\V_0 &= \frac{1}{3}(V_{ag} + V_{bg} + V_{cg}) \\&= \frac{1}{3}(277\angle 0^\circ + 260\angle -120^\circ + 295\angle 115^\circ) \\&= 15.912\angle 62.11^\circ \text{ volts}\end{aligned}$$

Part b)

$$\begin{aligned}I_1 &= \frac{V_1}{Z_{L1} + \frac{Z_\Delta}{3}} = \frac{277.1\angle -1.772^\circ}{10.73\angle 43.78^\circ} = 25.82\angle -45.55^\circ \text{ A} \\I_2 &= \frac{V_2}{Z_{L2} + \frac{Z_\Delta}{3}} = \frac{9.218\angle 216.59^\circ}{10.73\angle 43.78^\circ} = 0.8591\angle 172.81^\circ \text{ A} \\I_0 &= 0 \text{ A}\end{aligned}$$

Part c)

$$\begin{aligned} I_a &= 0 + 25.82\angle -45.55^\circ + 0.8591\angle 172.81^\circ \\ &= 25.15\angle -46.76^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} I_b &= 0 + (25.82\angle -45.55^\circ)(1\angle 240^\circ) + (0.8591\angle 172.81^\circ)(1\angle 120^\circ) \\ &= 25.71\angle 196.34^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} I_c &= 0 + (25.82\angle -45.55^\circ)(1\angle 120^\circ) + (0.8591\angle 172.81^\circ)(1\angle 240^\circ) \\ &= 26.62\angle 73.77^\circ \text{ A} \end{aligned}$$

3. A 3-phase transmission line has series reactance of X_s in all three phases and mutual inductance between every pair of phases of X_m . Voltages at one end of the line are V_a, V_b, V_c , and voltages at the other end of the line are V'_a, V'_b, V'_c . Unbalanced currents I_a, I_b, I_c flow in the phases.
- (a) Write a matrix equation $\underline{V}_{abc} - \underline{V}'_{abc} = \underline{Z}_{abc} \underline{I}_{abc}$ and substitute 012 quantities for $\underline{V}_{abc}, \underline{V}'_{abc}$, and \underline{I}_{abc} .
- (b) Determine the impedance matrix that relates the 012 voltages to the 012 currents.
- (c) Are the three sequence circuits coupled?

Part a)

$$\text{In abc:} \quad [V_{abc}] - [V'_{abc}] = [Z_{abc}][I_{abc}]$$

$$\text{In 012:} \quad [V_{012}] - [V'_{012}] = [Z_{012}][I_{012}]$$

Part b)

$$[Z_{012}] = [A]^{-1} [Z_{abc}] [A]$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} j \begin{bmatrix} X_s & X_m & X_m \\ X_m & X_s & X_m \\ X_m & X_m & X_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= \frac{1}{3} j \begin{bmatrix} X_s + 2X_m & X_s + 2X_m & X_s + 2X_m \\ X_s - X_m & aX_s + (1+a^2)X_m & a^2X_s + (1+a)X_m \\ X_s - X_m & a^2X_s + (1+a)X_m & aX_s + (1+a^2)X_m \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= j \begin{bmatrix} X_s + 2X_m & 0 & 0 \\ 0 & X_s - 2X_m & 0 \\ 0 & 0 & X_s - 2X_m \end{bmatrix}$$

Part c)

No, the mutual coupling has been eliminated.

4. A 3-phase transmission line has series reactance of X_s in all three phases and mutual inductances between phases of X_{ab} , X_{bc} , and X_{ca} . Everything else is the same as in problem 3. Repeat (a), (b), and (c) of problem 3.

Part a)

$$\text{In abc:} \quad [V_{abc}] - [V'_{abc}] = [Z_{abc}][I_{abc}]$$

$$\text{In 012:} \quad [V_{012}] - [V'_{012}] = [Z_{012}][I_{012}]$$

Part b)

$$[Z_{012}] = [A]^{-1} [Z_{abc}] [A]$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} j \begin{bmatrix} X_s & X_{ab} & X_{ca} \\ X_{ab} & X_s & X_{bc} \\ X_{ca} & X_{bc} & X_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= \frac{1}{3} j \begin{bmatrix} X_s + X_{ab} + X_{ca} & X_{ab} + X_s + X_{bc} & X_{ca} + X_{bc} + X_s \\ X_s + aX_{ab} + a^2X_{ca} & X_{ab} + aX_s + a^2X_{bc} & X_{ca} + aX_{bc} + a^2X_s \\ X_s + a^2X_{ab} + aX_{ca} & X_{ab} + a^2X_s + aX_{bc} & X_{ca} + a^2X_{bc} + aX_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= \frac{1}{3} j \begin{bmatrix} 3X_s + 2(X_{ab} + X_{bc} + X_{ca}) & (1+a^2)X_{ab} - X_{bc} + (1+a)X_{ca} & (1+a)X_{ab} - X_{bc} + (1+a^2)X_{ca} \\ (1+a)X_{ab} - X_{bc} + (1+a^2)X_{ca} & 3X_s - X_{ab} - X_{bc} - X_{ca} & 2(aX_{ab} + X_{bc} + a^2X_{ca}) \\ (1+a^2)X_{ab} - X_{bc} + (1+a)X_{ca} & 2(a^2X_{ab} + X_{bc} + aX_{ca}) & 3X_s - X_{ab} - X_{bc} - X_{ca} \end{bmatrix}$$

Part c)

Yes, the mutual coupling still exist between the phases (off-diagonal terms).

5. As you know, the power delivered to a three-phase network is given by

$$S = V_{ag}I_a^* + V_{bg}I_b^* + V_{cg}I_c^* = \underline{V}_{abc}^T \underline{I}_{abc}^*$$

Using the above relation, develop an expression for the power delivered to the three phase network in terms of only sequence quantities.

In matrix notation:

$$\begin{aligned} S_{3\phi} &= [\underline{V}_{abc}]^T [\underline{I}_{abc}]^* \\ &= \{[A][\underline{V}_{012}]\}^T \{[A][\underline{I}_{012}]\}^* \\ &= [\underline{V}_{012}]^T [A]^T [A]^* [\underline{I}_{012}]^* \end{aligned}$$

Now

$$\begin{aligned} [A]^T [A]^* &= \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \\ &= \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \end{aligned}$$

Therefore,

$$\begin{aligned} S_{3\phi} &= 3[\underline{V}_{012}]^T [\underline{I}_{012}]^* \\ &= 3[V_0 I_0^* + V_1 I_1^* + V_2 I_2^*] \end{aligned}$$