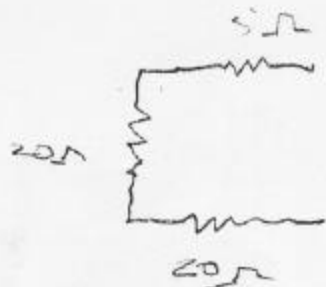
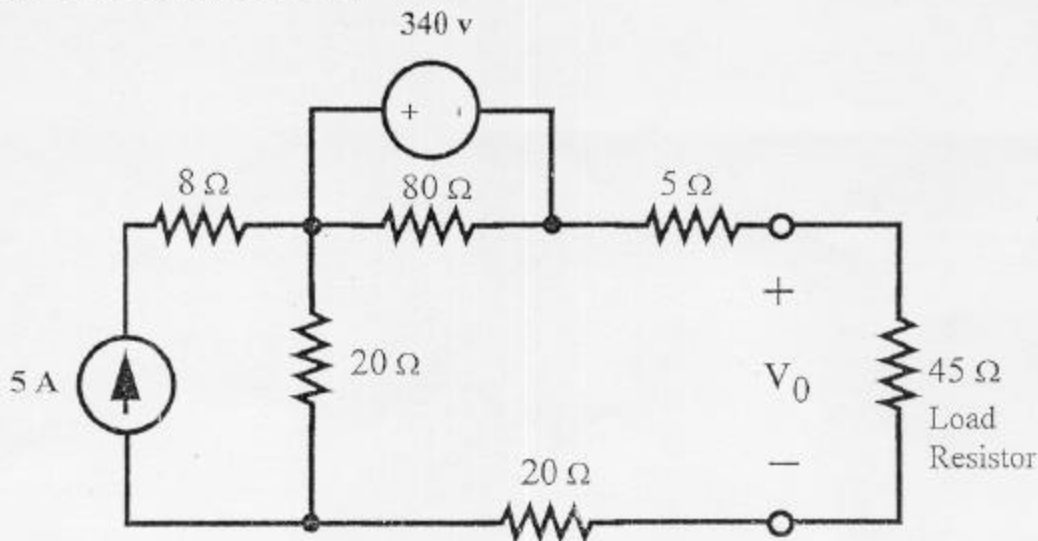

SOLUTIONS TO EXAM #2


1. For the circuit below: a) use superposition to find V_0 , b) is the value of the load resistor such that maximum power is being delivered to it?

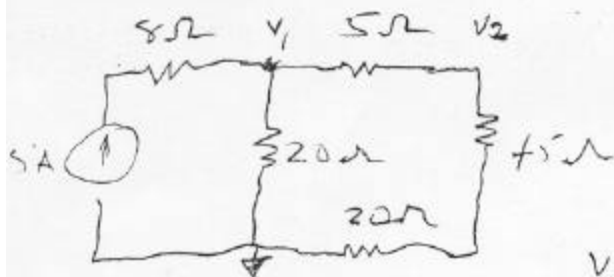4.54



$R_{th} = 45\Omega \rightarrow$ yes max power is being delivered to it.


$$-5 + \frac{V_1}{20} + \frac{V_1}{70} = 0 \quad V_1 = \frac{5}{\left(\frac{1}{20} + \frac{1}{70}\right)} = 77.78V$$



$$\rightarrow V_0' = \frac{77.78}{70} (45) = 50V$$

$$\frac{V_1}{20} + \frac{V_2}{70} + \frac{V_1 - V_2}{80} + \frac{V_2 - V_1}{80} = 0$$

$$V_2 = V_1 - 340$$

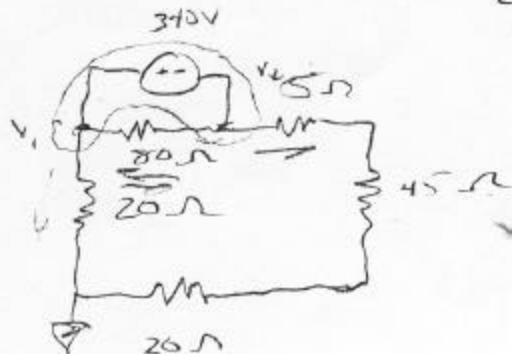


$$\rightarrow V_2 = -264.44V$$

$$V_0'' = \frac{V_2}{70} (45) = -170V \quad \therefore V_0 = V_0' + V_0'' = -120V$$

NAME: _____

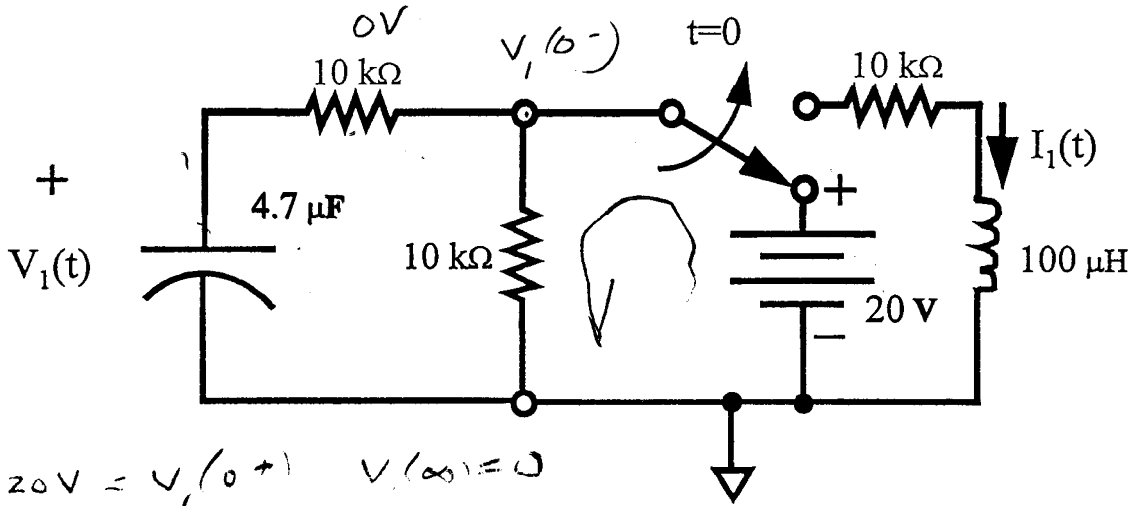2. In the circuit below, the switch has been in the bottom position for a long time. At $t=0$, the switch moves up to the top position. Please answer the following questions:
 What is $V_1(0^-)$? What is $V_1(0^+)$? What is $V_1(\infty)$?
 What is $I_1(0^-)$? What is $I_1(0^+)$? What is $I_1(\infty)$?




$$V_1(0^-) = 20\text{V} = V_1(0^+) \quad V_1(\infty) = 0$$


$$I_1(0^-) = 0 \quad I_1(0^+) \quad I_1(\infty) = 0$$

3. The switch in the circuit below has been open for a long time before closing at $t=0$. Find the voltage, $V_o(t)$ across the bottom inductor, for $t \geq 0+$. [HINT: source transformations will help.]

7.43

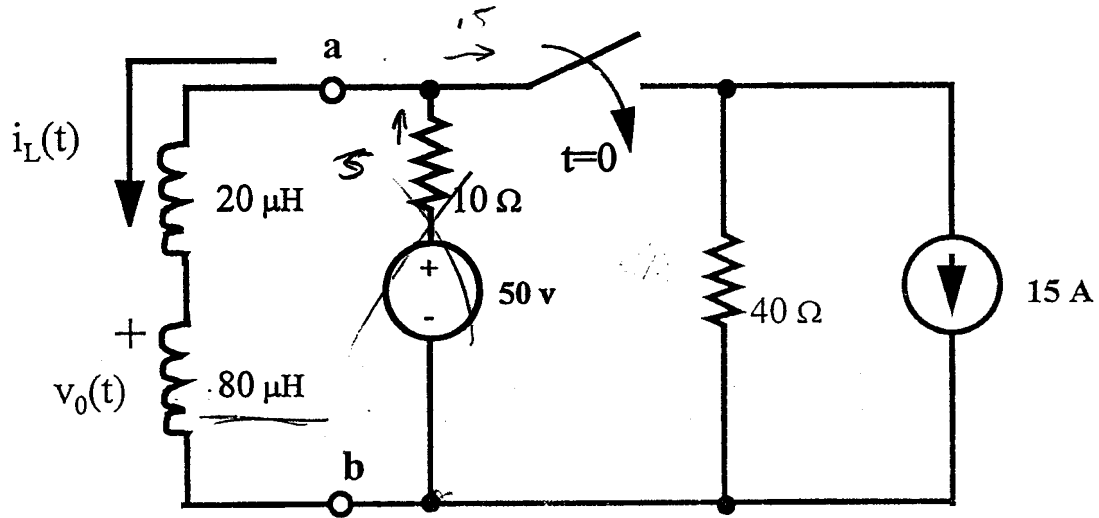

$5A \quad i_L \quad -10A$

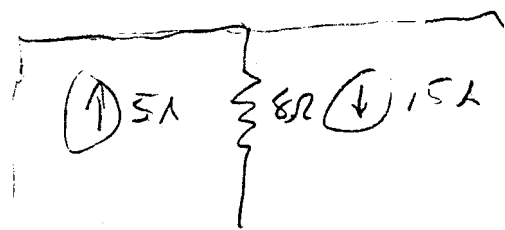

$+15 - 5 = 0 \rightarrow i_L = -10A$



$\tau = \frac{L_{eq}}{R_{th}} = \frac{80\mu H}{8\Omega} = (80,000)^{-1}$

$i_L(t) = -10 + (5 - (-10)) e^{-80,000t}$
 $10 + 15 e^{-80,000t}$

$V_o(t) = L \frac{di_L(t)}{dt} = 80\mu (15(-80,000)) e^{-80,000t}$
 $= -96 e^{-80,000t} V$

4. The energy stored in the capacitor in the circuit shown below is zero at the instant the switch is closed. a) Derive an equation for the output voltage, V_o , as a function of time. b) How many milliseconds does it take for the amplifier to reach saturation?

2.80

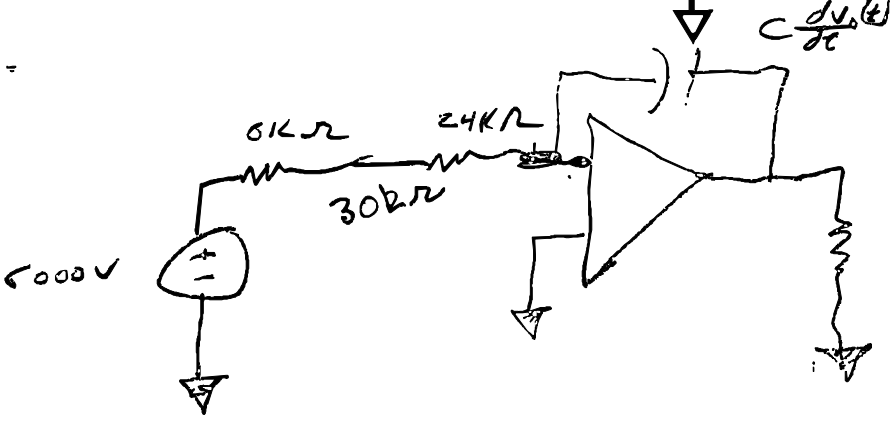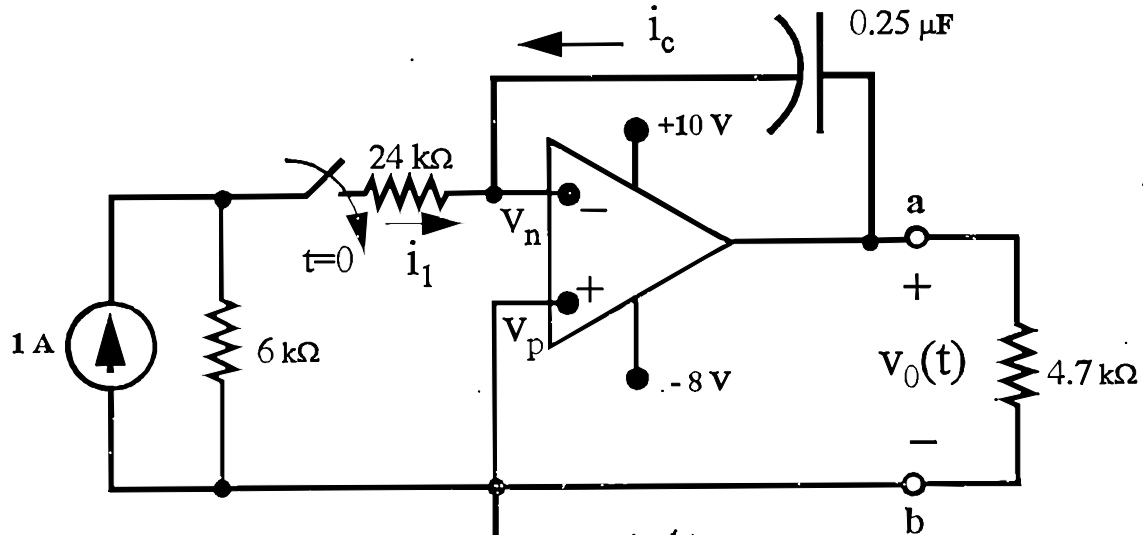

$$\frac{V_n - 5000}{30k\Omega} - C \frac{dV}{dt} = 0$$

$$C \frac{dV}{dt} = -\frac{5000}{30k}$$

$$\frac{dV}{dt} = -800000 \Rightarrow V_o(t) = \int_0^t -800000 dt = -800,000t$$

$$-800,000t = -8V \rightarrow$$

$$t = \frac{8}{800,000} = 10 \mu s$$